


## Part - B

1. Calculate


(i) Equivalent resistance across the terminal of the supply

(ii) Total current supplied by the source

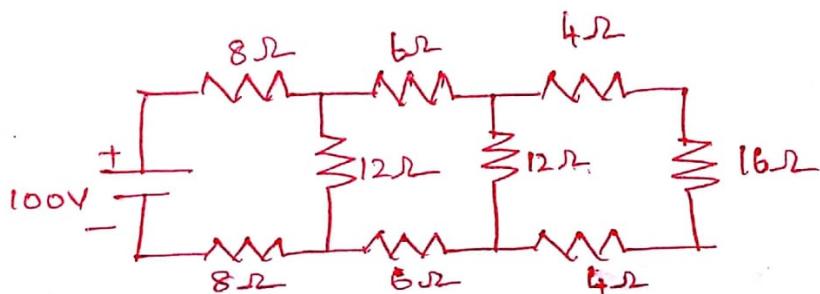(iii) Power delivered to  $16\Omega$  resistor in the circuit shown below




Sol

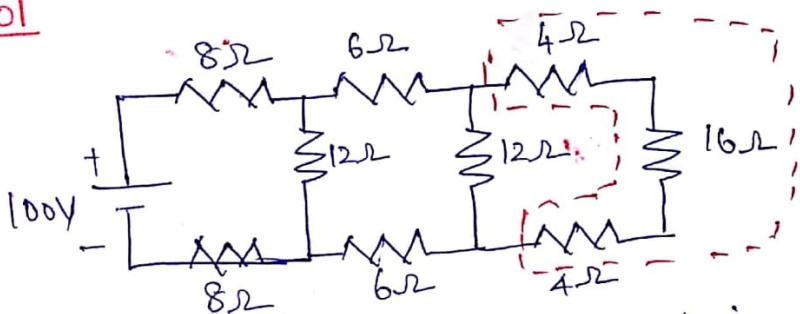


$4\Omega, 16\Omega, 4\Omega$  are connected in series

$$4 + 16 + 4 = 24 \Omega$$

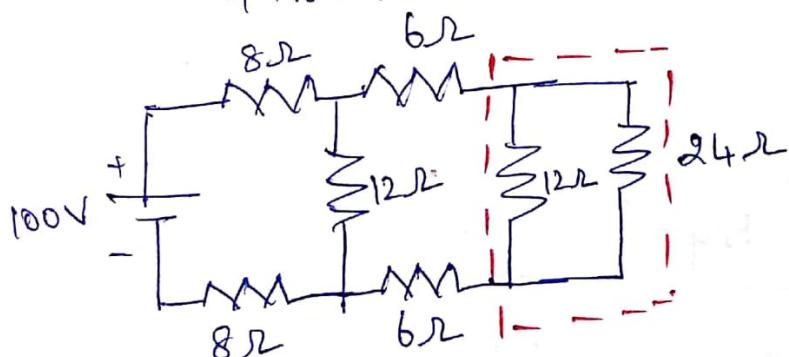


$12\Omega$  and  $24\Omega$  are connected in parallel
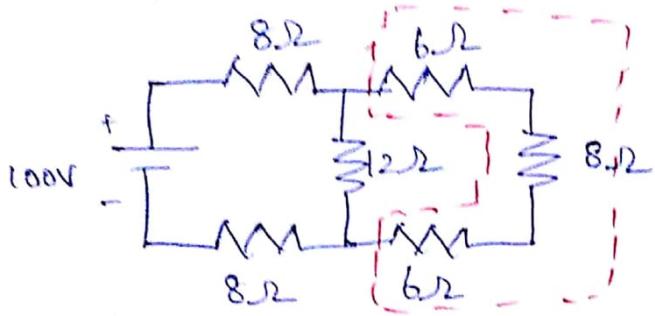
$$\frac{12 \times 24}{12 + 24} = 8\Omega$$




$6\Omega, 8\Omega, 6\Omega$  are connected in series

$$6 + 8 + 6 = 20\Omega$$

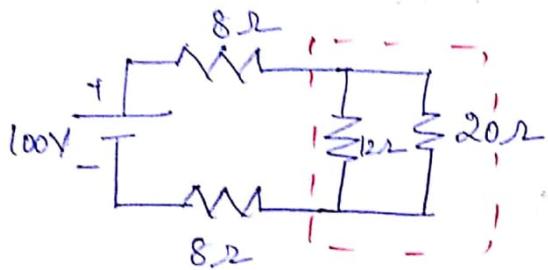


$12\Omega$  and  $20\Omega$  are connected in parallel
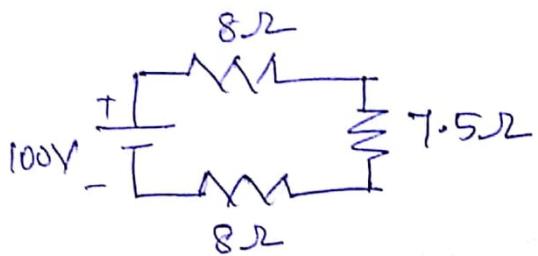
$$\frac{12 \times 20}{12 + 20} = 7.5\Omega$$




$8\Omega, 8\Omega, \& 7.5\Omega$  are connected in series

$$8 + 8 + 7.5 = 23.5\Omega$$

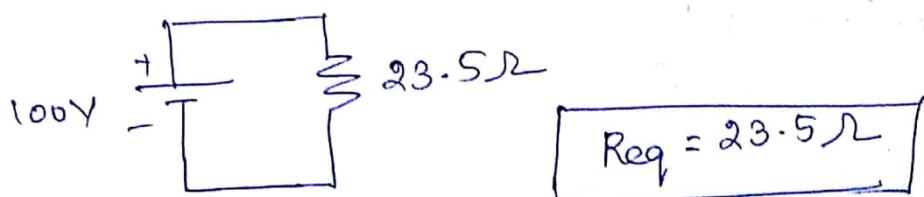

$$I = \frac{V}{R} = \frac{100}{23.5} = 4.25A$$

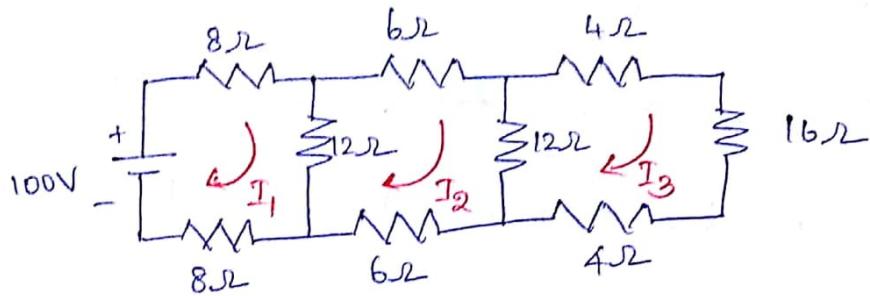Power delivered by  $16\Omega$  is  $P_{16\Omega} = I_{16\Omega}^2 R = I_3^2 R$  2



By KVL

$$\text{loop 1} \quad 8I_1 + 8I_1 + 12(I_1 - I_2) = 100$$

$$28I_1 - 12I_2 = 100 \rightarrow (1)$$

loop 2

$$6I_2 + 6I_2 + 12(I_2 - I_1) + 12(I_2 - I_3) = 0$$

$$-12I_1 + 36I_2 - 12I_3 = 0 \rightarrow (2)$$

loop 3

$$4I_3 + 4I_3 + 12(I_3 - I_2) + 16I_3 = 0$$

$$0I_1 - 12I_2 + 36I_3 = 0 \rightarrow (3)$$

Solving equation (1), (2) & (3)

$$I_1 = 4.25A$$

$$I_2 = 1.59A$$

$$I_3 = 0.5A$$


Power delivered by  $16\Omega$  is  $P_{16\Omega} = I_3^2 R = (0.5)^2 \cdot 16 = 4W$

$P_{16\Omega} = 4W$

Result:


- (i) Equivalent resistance  $R_{eq} = 23.5\Omega$
- (ii) Total current supplied by the battery  $I_T = 4.25A$
- (iii) Power delivered by  $16\Omega$  resistor  $P_{16\Omega} = 4W$

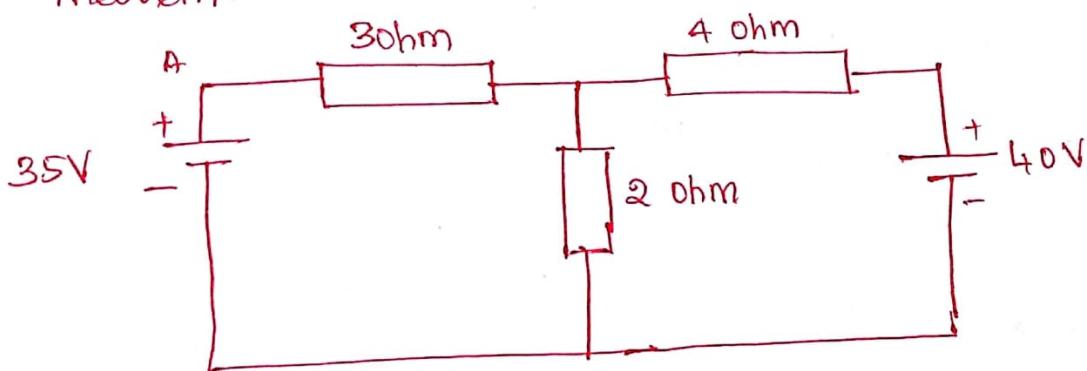2. Find the current in each branch using superposition theorem.



Sol

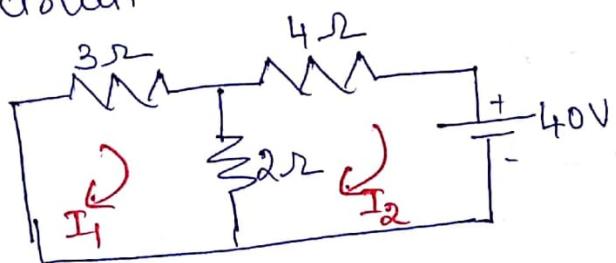(asdi)  
Short circuit the 35V battery and calculate  $I_1, I_2$



By KVL

$$\text{loop 1} \quad 3I_1 + 2(I_1 - I_2) = 0$$
$$5I_1 - 2I_2 = 0 \rightarrow (1)$$

loop 2,

$$4I_2 + 2(I_2 - I_1) = -40$$

$$-2I_1 + 6I_2 = -40 \rightarrow (2)$$

Solve the equations (1) & (2)

$$I_1 = -3.076 \text{ A}$$

$$I_2 = -7.69 \text{ A}$$

case (ii)

Short circuit the 40V battery & calculate  $I_1$  &  $I_2$



By KVL

loop 1

$$3I_1 + 2(I_1 - I_2) = 35$$

$$5I_1 - 2I_2 = 35 \rightarrow (1)$$

loop 2

$$4I_2 + 2(I_2 - I_1) = 0$$

$$-2I_1 + 6I_2 = 0 \rightarrow (2)$$

Solve eqn (1) & (2) & calculate  $I_1$  &  $I_2$

$$I_1 = 8.07 \text{ A}$$

$$I_2 = 2.69 \text{ A}$$

From both case(i) & case(ii)


$$I_1 = I_1 \text{ in case(i)} + I_1 \text{ in case(ii)}$$
$$= -3.706 + 8.076$$

$$I_1 = 4.37 A \quad \underline{\approx 5A} \quad \rightarrow (A)$$

$$I_2 = I_2 \text{ in case(i)} + I_2 \text{ in case(ii)}$$
$$= -7.69 + 2.69$$

$$I_2 = -5 A \quad \rightarrow (A)$$

case(iii)

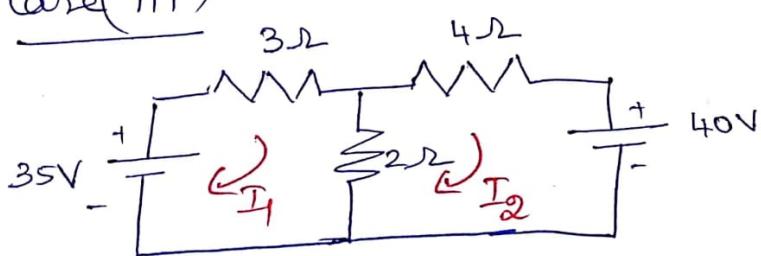

Apply KVL,

$$\text{loop 1} \quad 5I_1 - 2I_2 = 35 \quad \rightarrow (1)$$

$$\text{loop 2} \quad -2I_1 + 6I_2 = -40 \quad \rightarrow (2)$$

Solve eqn (1) & (2) we get

$$\begin{aligned} I_1 &= 5A \\ I_2 &= -5A \end{aligned} \quad \rightarrow (B)$$


$$\text{Eqn. (A)} = \text{Eqn. (B)}$$

Hence the superposition theorem is verified

3. Use Kirchoff's laws and find


4

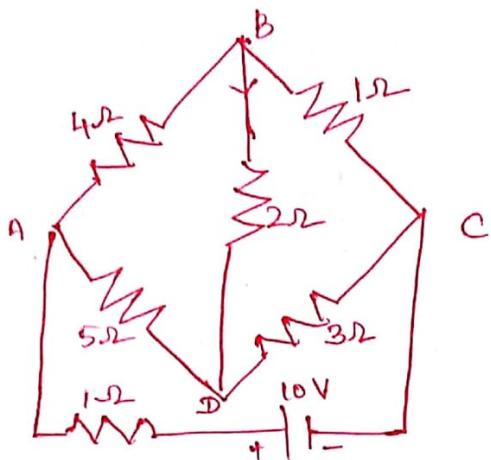- (i) calculate the current through  $1\Omega$  resistor (6)  
(ii) calculate the current through  $1\Omega$  resistor which is connecting series with battery (7)



Sol

Assume current direction

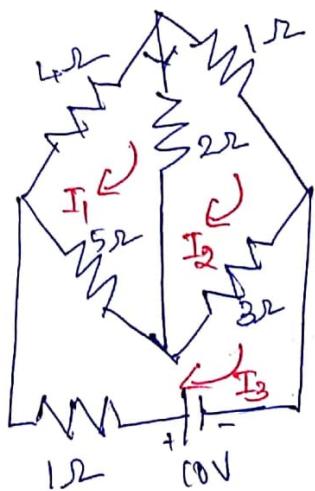

By KVL

$$\text{loop 1} \quad 11I_1 - 2I_2 - 5I_3 = 0 \rightarrow (1)$$

$$\text{loop 2} \quad -2I_1 + 6I_2 - 3I_3 = 0 \rightarrow (2)$$

$$\text{loop 3} \quad -5I_1 - 3I_2 + 9I_3 = 10 \rightarrow (3)$$

solving equation (1), (2) & (3) we get

$$I_1 = 1.45 \text{ A}$$

$$I_2 = 1.73 \text{ A}$$

$$I_3 = 2.49 \text{ A}$$

(i) Current through  $2\Omega$  resistor is  $I_{22} = I_2 - I_1$

$$= 1.73 - 1.45$$

$$\boxed{I_{22} = 0.28 \text{ A}}$$


(ii) Current through  $1\Omega$  resistor connecting series with the battery is  $I_3$

$$\therefore \boxed{I_3 = I_{12} = 2.49 \text{ A}}$$

4. For the following circuit find

(i) the current 'x' (10)

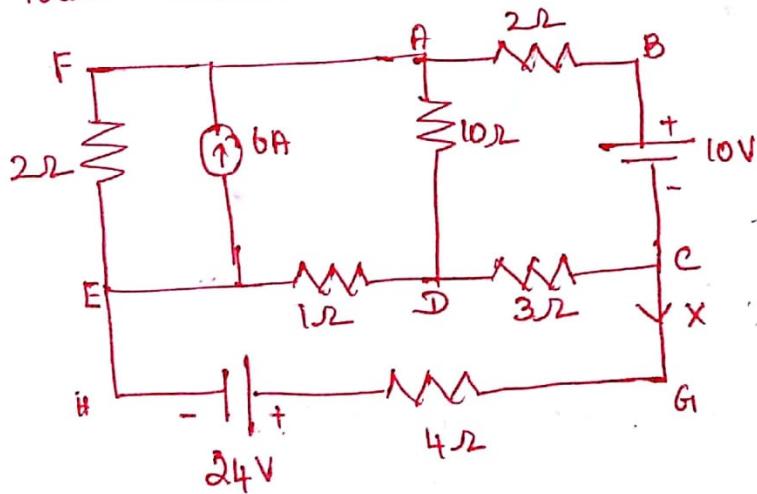(ii) Power across  $4\Omega$  resistor (3)




Sol

Transforming current source into equivalent voltage source,



$$V = IR = 6(2) = 12 \text{ V}$$

After source transformation,

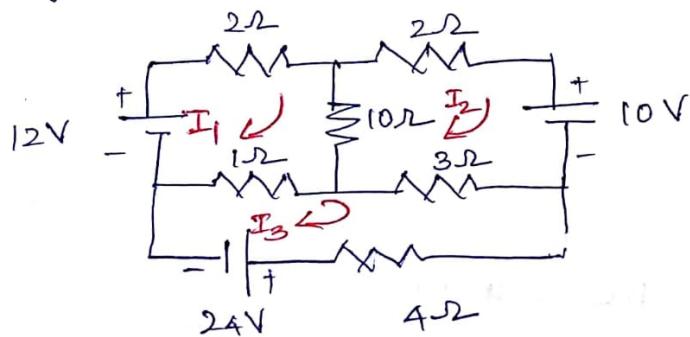

Apply KVL,

At loop 1,

$$13I_1 - 10I_2 - I_3 = 12 \rightarrow (1)$$

At loop 2,

$$-10I_1 + 15I_2 - 3I_3 = -10 \rightarrow (2)$$

loop 3,

$$-I_1 - 3I_2 + 8I_3 = -24 \rightarrow (3)$$

Solving eqn (1), (2) & (3) we get

$$I_1 = -1.02 \text{ A}$$

$I_1 = 1.02 \text{ A}$  (Assume opposite direction)

$$I_2 = -2.13 \text{ A}, \quad I_3 = -3.9 \text{ A}$$

(i) Current 'x' is  $I_3$

$$\therefore I_3 = x = -3.9 \text{ A} \quad [\text{direction is opposite to flow of current}]$$

(ii) Power across 4Ω resistor

$$P_{4\Omega} = (I_{4\Omega})^2 R = (I_3)^2 R = (-3.9)^2 \times 4$$
$$\boxed{P_{4\Omega} = 60.8 \text{ W}}$$

5. Explain Kirchoff's current and voltage laws with suitable examples (13)


(1) KVL - definition

Eg. problem - Find the solution

(2) KCL - definition


Eg - Problem - find the solution

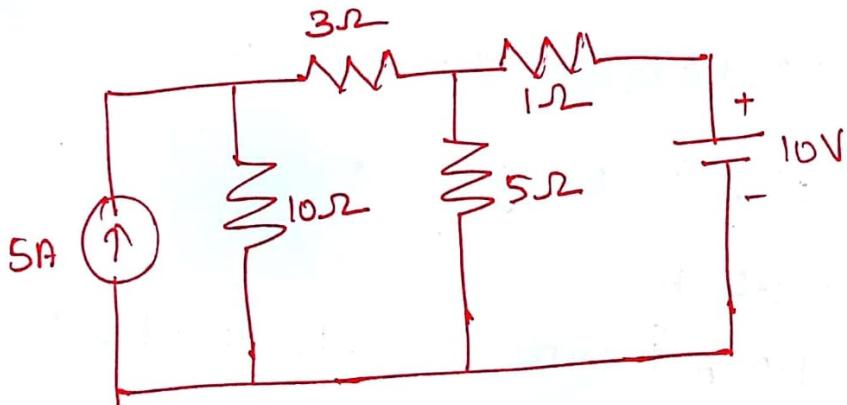6. Write the node voltage equations & determine the currents in each branch for the network shown (13)



Sol

6

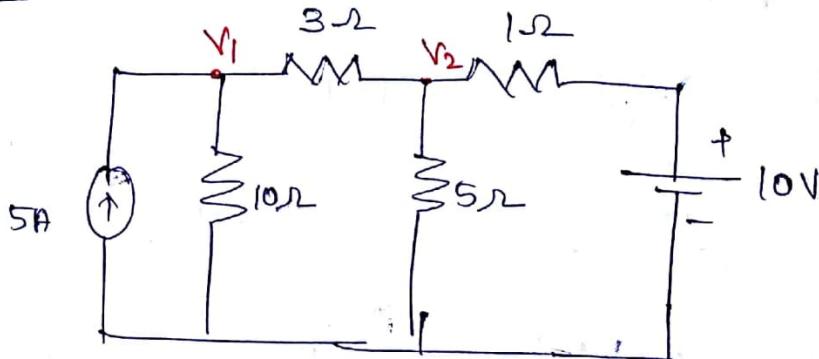

Apply KVL at node  $V_1$

$$\frac{V_1 - 0}{10} + \frac{V_1 - V_2}{3} = 5 \rightarrow (1)$$

$$\frac{V_1}{10} + \frac{V_1}{3} - \frac{V_2}{3} = 5$$

$$0.433V_1 - 0.33V_2 = 5 \rightarrow (2)$$

At node  $V_2$

$$\frac{V_2 - V_1}{3} + \frac{V_2}{5} + \frac{V_2 - 10}{1} = 0$$

$$\frac{-V_1}{3} + \frac{V_2}{3} + \frac{V_2}{5} + V_2 = 10$$

$$-0.33V_1 + 1.53V_2 = 10 \rightarrow (3)$$

Solving equations (2) & (3) we get

$$V_1 = 19.77V$$

$$V_2 = 10.8V$$


Currents in each branch are

$$I_{1,2} = \frac{V_1 - 0}{10} = \frac{19.95}{10} = 1.995 \text{ A}$$


$$I_{3,2} = \frac{V_1 - V_2}{3} = \frac{19.95 - 10.84}{3} = 3.04 \text{ A}$$

$$I_{1,2} = \frac{V_2 - 10}{1} = 10.08 - 10 = 0.84 \text{ A}$$

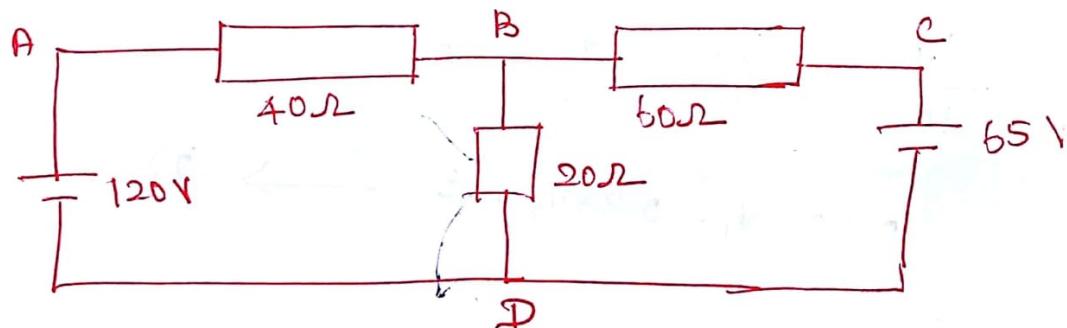7. In the circuit shown in figure, find the current in each branch using mesh analysis (13)



Sol

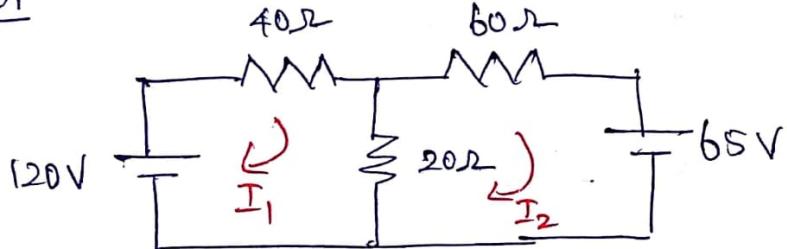

Apply KVL

$$\text{loop 1} \quad 40I_1 + 20(I_1 - I_2) = 120$$

$$60I_1 - 20I_2 = 120 \rightarrow (1)$$

loop 2

$$60I_2 + 20(I_2 - I_1) = -65$$

$$-20I_1 + 80I_2 = -65 \rightarrow (2)$$

Solving equations (1) & (2)

$$\begin{aligned} I_1 &= 1.886 \text{ A} \\ I_2 &= -0.34 \text{ A} \end{aligned}$$

$$\begin{bmatrix} 60 & -20 \\ -20 & 80 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 120 \\ -65 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 60 & -20 \\ -20 & 80 \end{vmatrix} = (60)(80) - (-20)(-20) = 4400$$

$$\Delta_1 = \begin{vmatrix} 120 & -20 \\ -65 & 80 \end{vmatrix} = (120)(80) - (-65)(-20) \\ = 8300$$

$$\Delta_2 = \begin{vmatrix} 60 & 120 \\ -20 & -65 \end{vmatrix} = (60)(-65) - (120)(-20) = -1500$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{8300}{4400} = 1.886 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-1500}{4400} = -0.34 \text{ A}$$


Result

$$I_1 = 1.886 \text{ A}$$


$$I_2 = -0.34 \text{ A}$$

8. Determine the current in  $10\Omega$  resistor using  
Thevenin's theorem (13).

Step 1

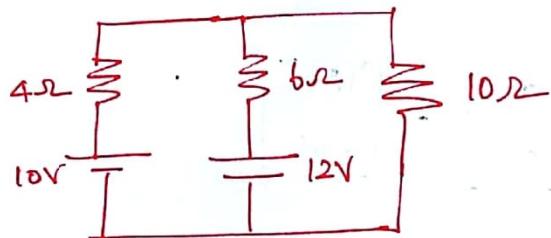


Sol

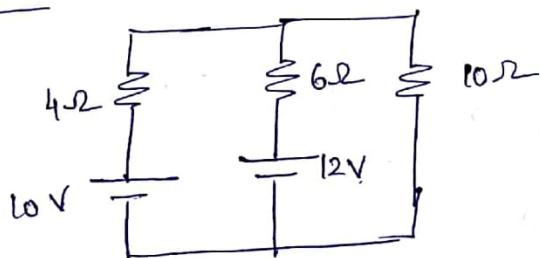


Step 1

Remove the load resistor  $10\Omega$

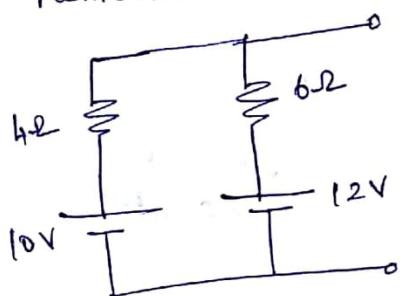

Step 2

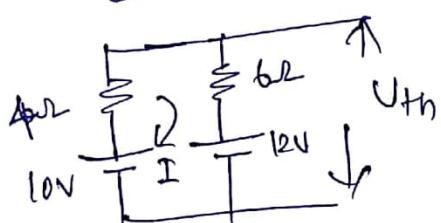Determine thevenin's voltage ( $V_{th}$ )




$$\text{By KVL, } 4I + 6I = 10 - 12$$

$$10I = -2$$

$$I = -0.2 \text{ A}$$

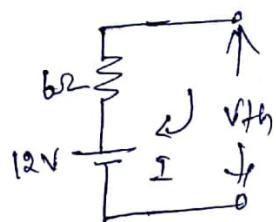current in  $6\Omega$  resistor is  $-0.2A$



By KVL

$$6I = 12 - V_{th}$$

$$V_{th} = 12 - 6I = 12 - 6(0.2)$$

$$\boxed{V_{th} = 10.8 \text{ V}}$$


Step 3:

To find  $R_{th}$

- open circuit the ~~left side~~ current source

- short circuit the voltage source

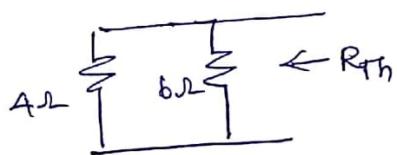$4\Omega$  &  $6\Omega$  are connected in parallel




$$\frac{4 \times 6}{4 + 6} = 2.4\Omega$$

Step 4

Thevenin's equivalent circuit,

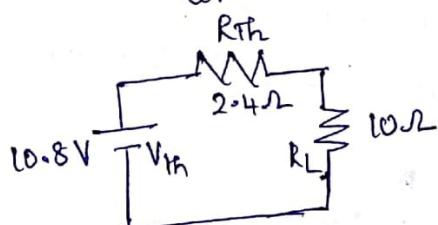Connect  $R_{th}$  in series with  $V_{th}$  & reconnect the load resistor




Step 5 To find load current

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{10.8}{2.4 + 10} = 0.871 \text{ A}$$


$$V_L = I_L \times R_L = 0.871 \times 10 = 8.7 \text{ V}$$

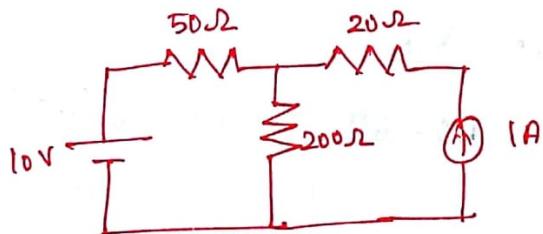9. Determine the voltage across  $20\Omega$  resistor in the circuit, using norton's theorem (13)



Sol short the load resistor  $20\Omega$  & find the norton's current ( $I_N$ )

Step1

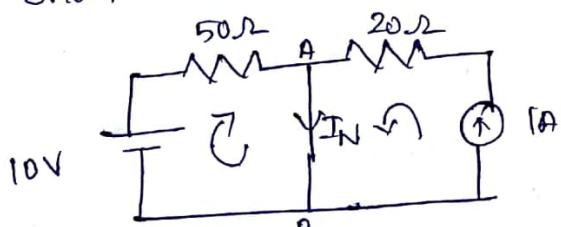

$$\text{Due to } 10V \text{ source } I_{N10V} = \frac{V}{R} = \frac{10}{50} = 0.2A$$


$$\text{Due to } 1A \text{ source } I_{1A} = 1A$$

$$\text{Total current through } I_N = I_{N10V} + I_{1A} = 0.2 + 1$$

$$I_N = 1.2A$$


Step2 find  $R_N$  — Open circuit the current source &

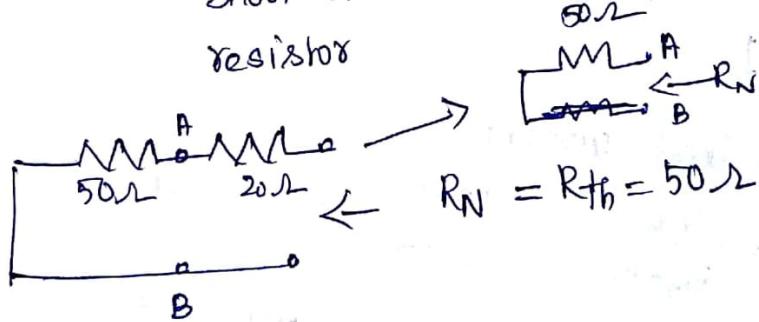Short circuit the voltage source & remove load  
resistor



Step 3

Norton's equivalent circuit

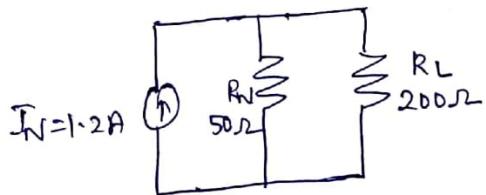

Step 4

$$I_L = \frac{I_N R_N}{R_N + R_L} = \frac{1.2 \times 50}{50 + 200}$$


$$I_L = 0.24 \text{ A}$$

$$V_L = I_L R_L = 0.24 \times 200$$

$$V_L = 48 \text{ V}$$


10(i) Draw the Thévenin's equivalent circuit for the following circuit (7)

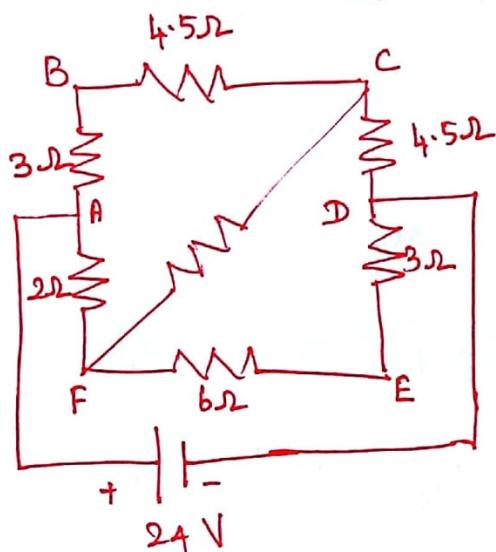(ii) Determine the current through the branch FE (6)




### Step 1

Remove the load resistor  $5\Omega$

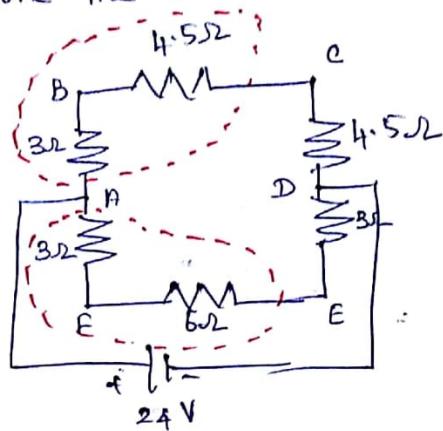

$4.5\Omega$  &  $3\Omega$  are connected in series  $4.5 + 3 = 7.5\Omega$

$6\Omega$  &  $3\Omega$  are " " "

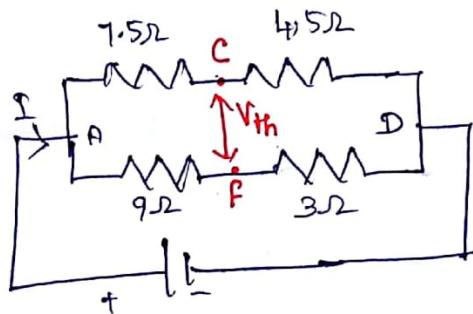

### Step 2

Potential at point C w.r.t. the negative terminal of the battery

Apply voltage division rule,

$$V_C = \frac{24 \times 4.5}{4.5 + 7.5} = 9V$$

$$V_F = \frac{24 \times 9}{9 + 3} = 18V$$

$$V_{th} = V_{FC} = V_F - V_C = 18 - 9$$


$$\boxed{V_{th} = 9V}$$

Step 3


10

To find  $R_{Th}$

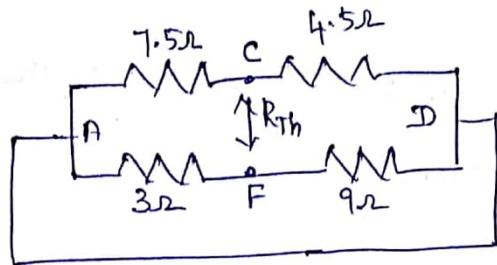Open the current source, short the voltage source & remove the load resistor



Redraw the above circuit

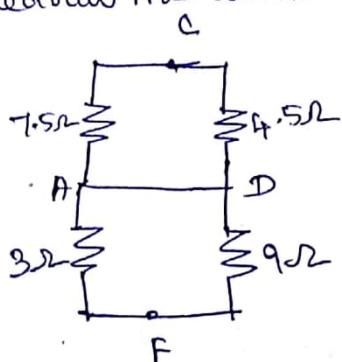


$7.5\Omega$  &  $4.5\Omega$  are in parallel

$$\frac{7.5 \times 4.5}{7.5 + 4.5} = 2.8\Omega$$

$3\Omega$  &  $9\Omega$  are in parallel

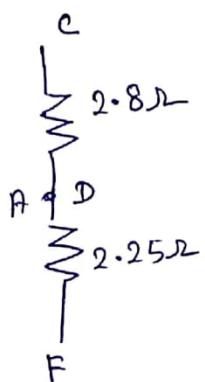
$$\frac{3 \times 9}{3 + 9} = 2.25\Omega$$



$2.8\Omega$ ,  $2.25\Omega$  are in series

$$2.8 + 2.25 = 5.06\Omega$$

Step 4 Thevenin's equivalent circuit

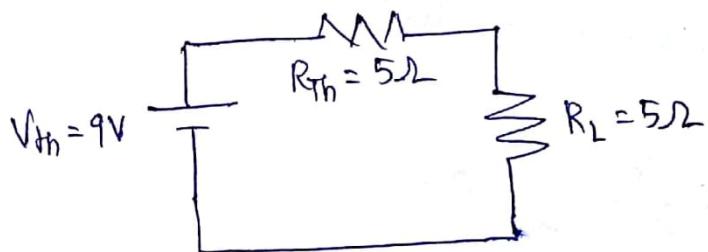


Step 5

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{9}{5.06 + 5} = 0.9 \text{ A}$$


$$V_L = I_L R_L = 0.9 \times 5 = 4.5 \text{ V}$$

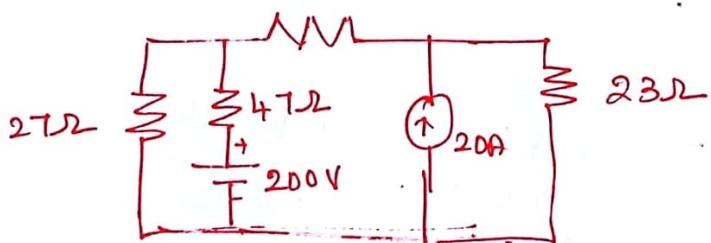11. Compare the current through  $23\Omega$  resistor of the figure below using superposition theorem.



Sol

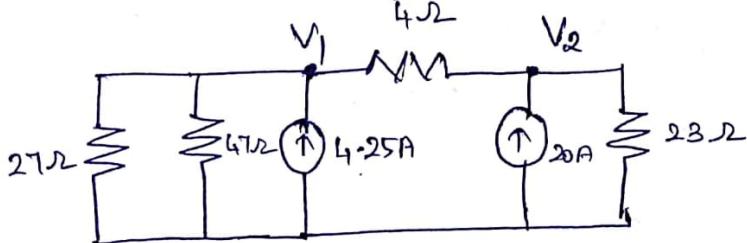using node voltage analysis  
convert the voltage source to current source



At node  $V_1$

$$\frac{V_1}{27} + \frac{V_1}{47} + \frac{V_1 - V_2}{4} = 4.25 \quad \rightarrow (1)$$

$$0.308V_1 - 0.25V_2 = 4.25$$

At node  $V_2$

$$\frac{V_2}{23} + \frac{V_2 - V_1}{4} = 20$$

$$-0.25V_1 + 0.29V_2 = 20 \quad \rightarrow (2)$$

Solving eqn. (1) & (2)

$$V_1 = 232 \cdot 38 \text{ V}$$

$$V_2 = 269 \cdot 29 \text{ V}$$

Current through  $23\Omega$  resistor  $I_{23\Omega} = \frac{V_2}{R} = \frac{V_2}{23}$


$$= \frac{269 \cdot 29}{23}$$

$I_{23\Omega} = 11.708 \text{ A}$

$\rightarrow (1)$


Case(i)

open circuit the current source

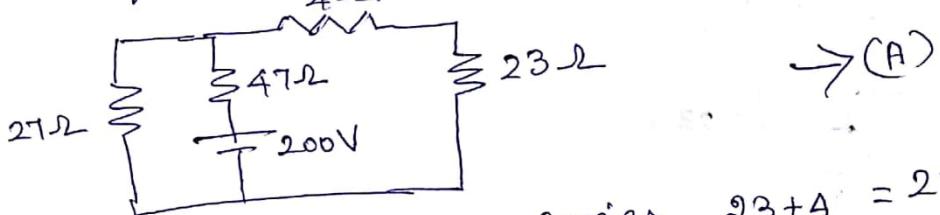


$\rightarrow (A)$

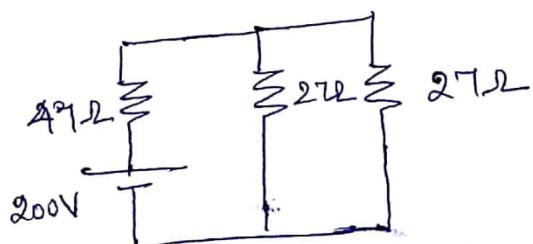$23\Omega$  &  $4\Omega$  are in series  $23+4 = 27\Omega$




$27\Omega$  &  $27\Omega$  are in parallel
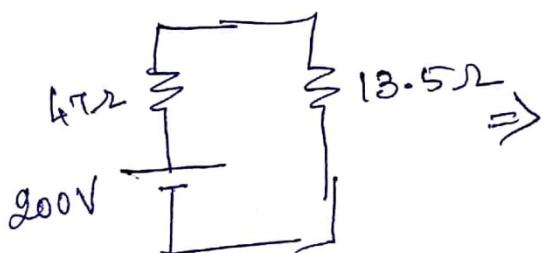
$$\frac{27 \times 27}{27 + 27} = 13.5\Omega$$



$13.5\Omega$  &  $47\Omega$  are in series

$$13.5 + 47 = 60.5\Omega$$

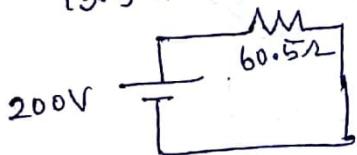

$$\therefore \text{Total current } I_T = \frac{V}{R} = \frac{200}{60.5} = 3.3 \text{ A}$$

For the circuit (A)

Current through  $23\Omega$  resistor is

Apply current division rule

$$I_{23\Omega} = \frac{3.3 \times 27}{23 + 4 + 27} =$$

$$I_{23\Omega} = 1.65 \text{ A} \quad \text{due to } 200\text{V source}$$


Case ii

Short circuit the voltage source




$47\Omega$  &  $23\Omega$  are in parallel
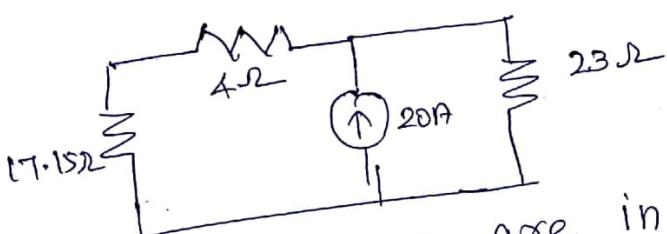
$$\frac{27 \times 47}{27 + 47} = 17.15 \Omega$$



$17.15\Omega$  and  $4\Omega$  are in series

~~$17.15 + 4 = 21.15\Omega$~~

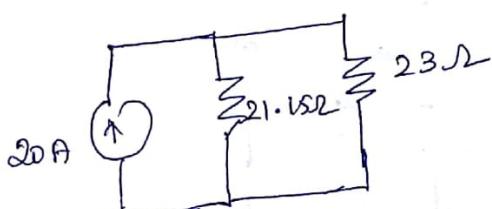

Current through  $23\Omega$  resistor due to  $20V$

current source is

$$I_{23\Omega} = \frac{20}{23 + 23} \times 21.15$$

$$\boxed{I_{23\Omega} = 9.58A}$$
 due to current source

Total current through  $23\Omega$  resistor

$$= \text{current through } 23\Omega \text{ resistor by voltage source due to } + \text{ current source}$$


$$= 1.65 + 9.58$$

$$\boxed{I_{23\Omega} = 11.23 A} \rightarrow (2)$$

$$\text{eqn (1)} = (2)$$


Hence superposition theorem is verified.

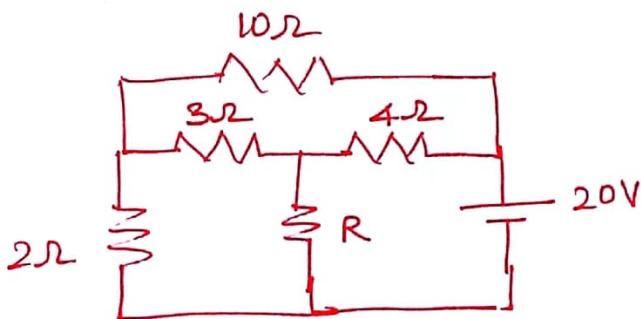12. Obtain the Norton's equivalent circuit across the unknown resistor 'R': (13)



Sol

Step 1  
Remove load resistor

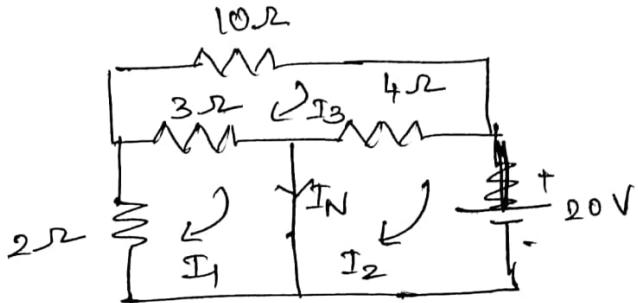

To find  $I_N$

By KVL

loop 1  $2I_1 + 3(I_1 - I_3) = 0 \rightarrow (1)$

$$2I_1 - 3I_3 = 0$$

loop 2  $4(I_2 - I_3) = -20 \rightarrow (2)$

$$4I_2 - 4I_3 = -20 \rightarrow (2)$$

loop 3  $10I_3 + 3(I_3 - I_1) + 4(I_3 - I_2) = 0 \rightarrow (3)$

$$-3I_1 - 4I_2 + 17I_3 = 0$$

Solving (1), (2) & (3)

$$I_1 = -1.07A$$

$$I_2 = -6.78A$$

$$I_3 = -1.78A$$




$$I_N = I_1 - I_2 \\ = -1.07 - (-6.78)$$

$$I_N = 5.72 \text{ A}$$

Step 2


To find  $R_{th}$

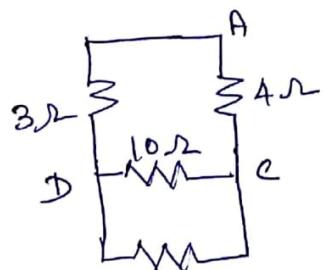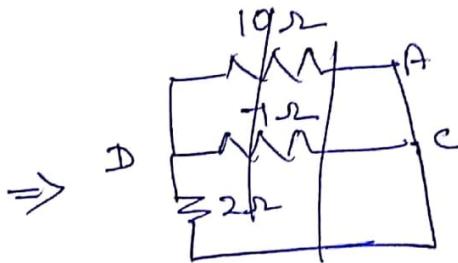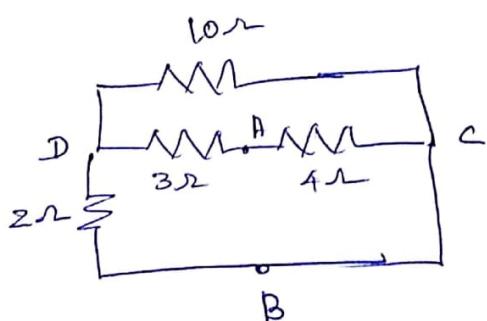short circuit the voltage source, open circuit the current source and remove load resistor.



$2\Omega$  &  $10\Omega$  are in parallel
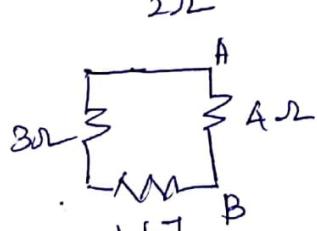
$$\frac{2 \times 10}{2 + 10} = 1.67\Omega$$



$3\Omega$  &  $1.67\Omega$   $\Rightarrow$  Series

$$3 + 1.67 = 4.67\Omega$$




$4.67\Omega$  &  $4\Omega$   $\Rightarrow$  parallel


$$\frac{4.67 \times 4}{4.67 + 4} = 2.15\Omega$$

Step 3

Norton's equivalent circuit

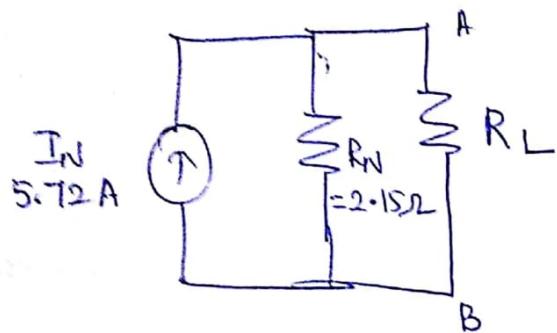


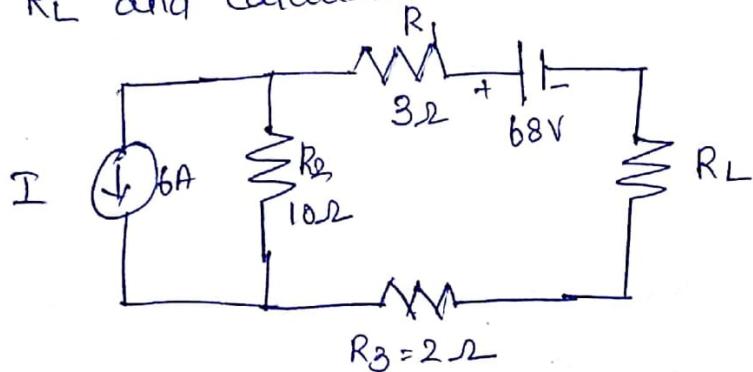- 13) Find the value  $R_L$  in the fig. for maximum power  
to  $R_L$  and calculate the maximum power.



Sol

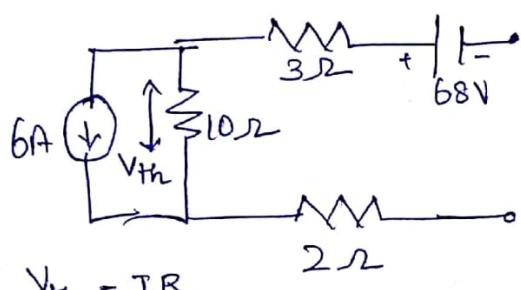
To find the  $V_{th}$ , open the load resistance  $R_L$ .



$$V_{th} = IR$$

$$V_{th} = 6(10) = 60V$$

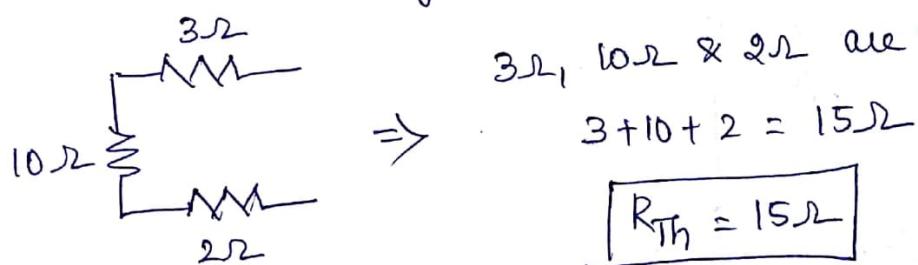To find  $R_{th}$  : Open current source, short circuit the voltage source and open  $R_L$



$$P_{max} = \frac{(V_{th})^2}{4R_{th}} = \frac{(60)^2}{4 \times 15} = \frac{3600}{60}$$


$$\boxed{P_{max} = 60W}$$

Result:

$$R_L = 15\Omega$$

$$P_{\max} = 60W$$

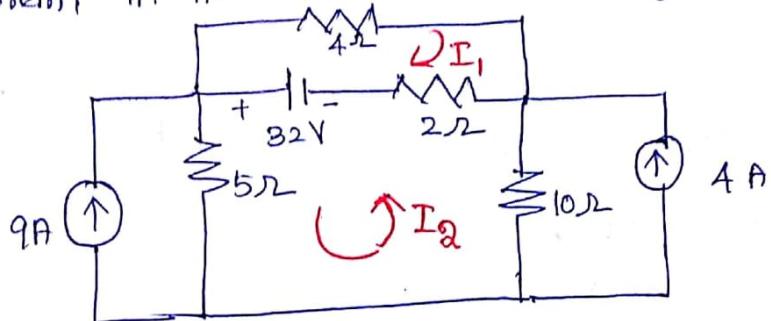14. Estimate the current through  $5\Omega$  resistor using superposition theorem, in the circuit shown in fig.




SOL

Case(i)

9A current source is active and  
4A & 32V are inactive


32V - Short circuit

4A - Open circuit

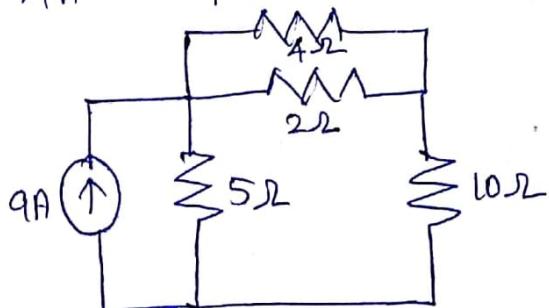


4Ω and 2Ω are connected in parallel
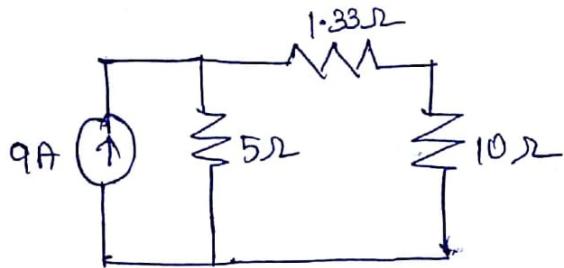
$$\frac{4 \times 2}{4+2} = \frac{8}{6} = 1.33\Omega$$



$1.33\Omega$  &  $10\Omega$  are connected in Series

$$1.33 + 10 = 11.33\Omega$$

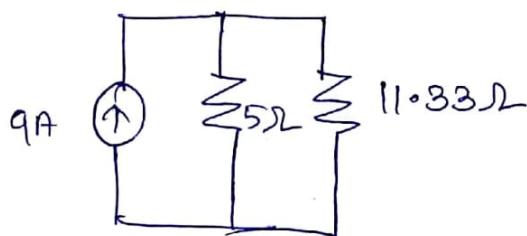

Current through  $5\Omega$  resistor due to  $9A$  source  $I'$

Using current division rule,

$$I' = I_{5\Omega} = \frac{9 \times 11.33}{5 + 11.33}$$

$$= \frac{101.97}{16.33} = 6.24 \text{ A}$$

$I' = I_{5\Omega} = 6.24 \text{ A}$


Downwards

Case(ii)

32V voltage source is active

9A & 4A current sources are inactive

9A & 4A  $\Rightarrow$  open circuit

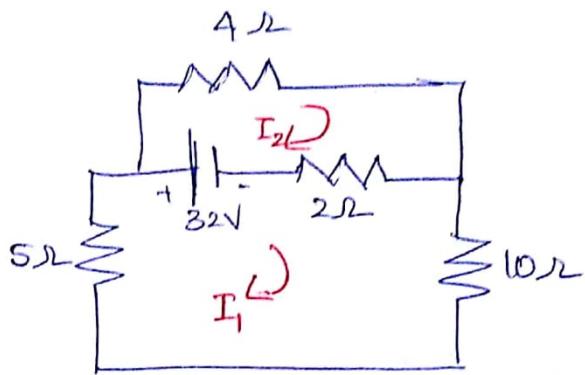

Apply KVL,

loop 1,

$$5I_1 + 10I_1 + 2(I_1 - I_2) = -32$$

$$17I_1 - 2I_2 = -32 \rightarrow (1)$$

loop 2,

$$4I_2 + 2(I_2 - I_1) = 32$$

$$-2I_1 + 6I_2 = 32 \rightarrow (2)$$

$$I_1 = -1.306 \text{ A}$$

$$I_2 = 4.89 \text{ A}$$

Current through  $5\Omega$  resistor is  $I_1$

$$I_{5\Omega} = I_1 = -1.306 \text{ A} \text{ upwards}$$

Current through  $5\Omega$  resistor due to  $32V$  voltage source is  $I''$

$$I'' = I_{5\Omega} = -1.306 \text{ A} \text{ upwards}$$


Case(iii)

4A current source is active

32V & 9A are inactive


9A  $\rightarrow$  open circuit

32V  $\rightarrow$  short circuit

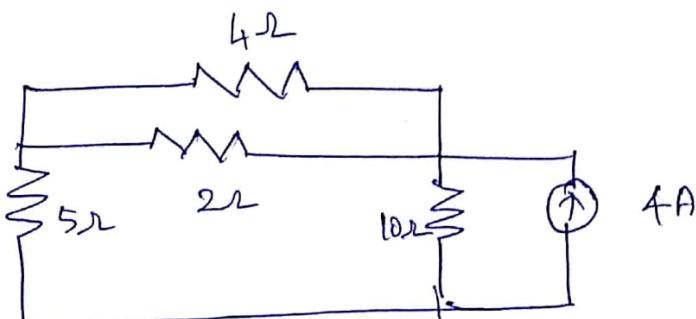

4Ω & 2Ω are connected in parallel
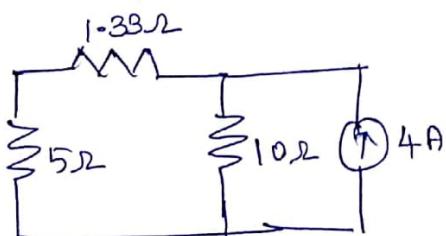
$$\frac{4 \times 2}{4+2} = \frac{8}{6} = 1.33\Omega$$



Using current division rule,

Current through 5Ω resistor due to 4A current source is  $I'$

$$I''' = I_{5\Omega} = \frac{4 \times 10}{5 + 10 + 1.33} = \frac{40}{16.33}$$

$I''' = I_{5\Omega} = 2.449 \text{ A} \quad \text{Downwards}$

Total current through 5Ω resistor  $I = I' + I'' + I'''$

$$= 6.24 - 1.306 + 2.449$$

$I_{5\Omega} = 7.383 \text{ A}$

## Result

Current through  $S_2$  resistor  $I_{S2} = 7.383 \text{ A}$